

Name: Ayesha Ahmad


EE-272L Digital Systems Design

Reg. No. : 2021-EE-052

Marks Obtained: _____

Lab Manual 3

Combinational Circuit Design using Vivado

 

Question 1

Part A

A	B	C	$O = \bar{C}$	$R = P = A + B$	$Q = AB$	$S = \bar{Q}\bar{R}$	$X = O \oplus P$	$Y = P \oplus S$
0	0	0	1	0	0	1	1	1
0	0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	1	1	0
1	0	0	1	1	0	1	0	0
1	0	1	0	1	0	1	1	0
1	1	0	1	1	1	0	0	1
1	1	1	0	1	1	0	1	1

Part B

The maximum combinational delay is from b to y with a time delay of 6.771ns.

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	2	b	y	6.771	5.165	1.606	∞	input port clock
Path 2	∞	3	2	1	c	x	6.735	5.130	1.606	∞	input port clock

Part C

It used 2 LUTs and 5 IOs; 3 of which are for inputs and 2 for outputs.

Ref Name	Used	Functional Category
IBUF	3	IO
OBUF	2	IO
LUT3	1	LUT
LUT2	1	LUT

Question 2

```
`timescale 1ns / 1ps
```

```
module task1(output logic x,y,
```

```
input logic a,b,c
```

```
);
```

```
assign x = (a | b) ^ ~c;
```

```
assign y = (a | b) ^ (a & b) ~& (a | b);
```

```
endmodule
```