

Name: Ayesha Ahmad

EE-272L Digital Systems Design

Reg. No. : 2021-EE-052

Marks Obtained: \_\_\_\_\_

## Lab Manual 4b

### Combinational Circuit Design using K-Maps

#### Question 1

##### Part A

Select which number to display:

a	b	c	d	Character	Seg.A	Seg.B	Seg.C	Seg. D	Seg.E	Seg.F	Seg.G	DP
0	0	0	0	0	0	0	0	0	0	0	1	1
0	0	0	1	1	1	0	0	1	1	1	1	1
0	0	1	0	2	0	0	1	0	0	1	0	1
0	0	1	1	3	0	0	0	0	1	1	0	1
0	1	0	0	4	1	0	0	1	1	0	0	1
0	1	0	1	5	0	1	0	0	1	0	0	1
0	1	1	0	6	0	1	0	0	0	0	0	1
0	1	1	1	7	0	0	0	1	1	1	1	1
1	0	0	0	8	0	0	0	0	0	0	0	1
1	0	0	1	9	0	0	0	0	1	0	0	1
1	0	1	0	A	0	0	0	1	0	0	0	1
1	0	1	1	B	1	1	0	0	0	0	0	1
1	1	0	0	C	0	1	1	0	0	0	1	1
1	1	0	1	D	1	0	0	0	0	1	0	1
1	1	1	0	E	0	1	1	0	0	0	0	1
1	1	1	1	F	0	1	1	1	0	0	0	1

Select which 7-segment to display on:

x	y	z	AN0	AN1	AN2	AN3	AN4	AN5	AN6	AN7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

## Part B

$$A = \overline{a}\overline{b}\overline{c}d + \overline{a}b\overline{c}d + ab\overline{c}d + abcd$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	0	1	0	0
10	0	0	1	0

$$B = \overline{a}\overline{b}cd + ab\overline{c}d + acd + bc\overline{d}$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	1	0	1	1
10	0	0	1	0

$$C = ab\overline{c}d + abc + \overline{a}b\overline{c}d$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	1	0	1	1
10	0	0	0	0

$$D = \overline{a}\overline{b}cd + \overline{a}b\overline{c}d + ab\overline{c}d + bcd$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	0	0	1	0
10	0	0	0	1

$$E = \overline{a}b\overline{c} + \overline{b}cd + \overline{a}d$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	1	1	0
01	1	1	1	0
11	0	0	0	0
10	0	1	0	0

$$F = ab\overline{c}d + \overline{a}b\overline{c}d + \overline{a}bc + \overline{a}cd$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	1	0	0
10	0	0	0	0

$$G = \overline{a}b\overline{c} + \overline{a}bcd + ab\overline{c}d$$

$\begin{array}{c c} c & d \\ \hline a & b \end{array}$	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	1	0	0	0
10	0	0	0	0

$$AN0 = \overline{x}\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	1	0
01	0	0
11	0	0
10	0	0

$$AN1 = \overline{x}\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	1
01	0	0
11	0	0
10	0	0

$$AN2 = \overline{x}\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	1	0
11	0	0
10	0	0

$$AN3 = \overline{x}\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	0	1
11	0	0
10	0	0

$$AN4 = x\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	0	0
11	0	0
10	1	0

$$AN5 = x\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	0	0
11	0	0
10	0	1


$$AN6 = x\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	0	0
11	1	0
10	0	0

$$AN7 = x\overline{y}z$$

$\begin{array}{c c} z \\ \hline x & y \end{array}$	0	1
00	0	0
01	0	0
11	0	1
10	0	0


## Part C

 
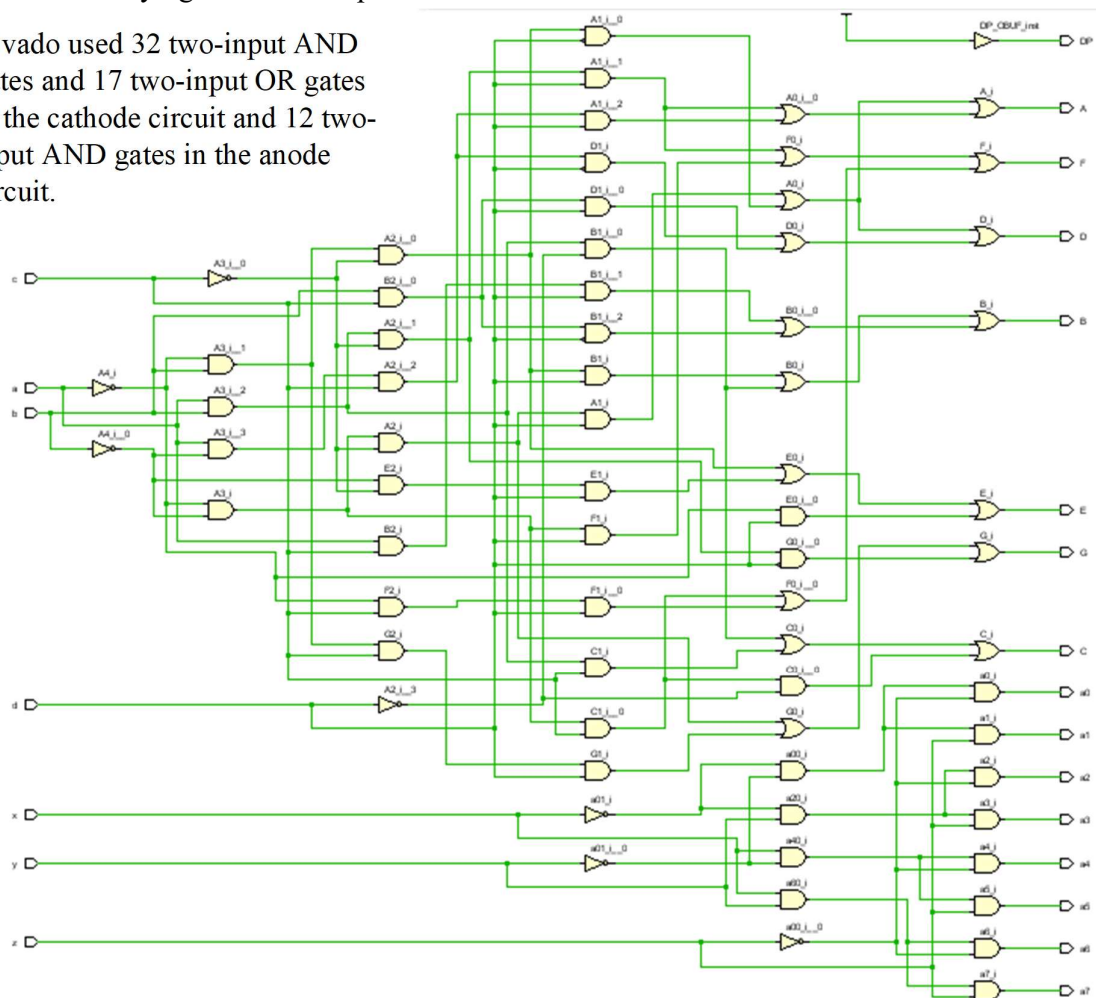
## Part D

Vivado only used two-input gates: 44 AND and 17 OR gate. Mine has 33 AND and 7 OR gates with varying number of inputs.

Vivado used 32 two-input AND gates and 17 two-input OR gates in the cathode circuit and 12 two-input AND gates in the anode circuit.



My circuit has the following list of AND gates: 2 two-input, 12 three-input and 12 four-input, and OR gates: 3 three-input and 4 four-input, in the cathode circuit. And 8 three-input AND gates in the anode circuit.

## Part E

The maximum delay in Synthesis is from x to a2 of 6.851ns.

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	8	x	a2	6.851	5.246	1.606	∞	input port clock
Path 2	∞	3	2	8	x	a7	6.832	5.227	1.606	∞	input port clock
Path 3	∞	3	2	8	x	a3	6.829	5.223	1.606	∞	input port clock
Path 4	∞	3	2	8	z	a5	6.805	5.200	1.606	∞	input port clock
Path 5	∞	3	2	8	z	a4	6.804	5.198	1.606	∞	input port clock
Path 6	∞	3	2	7	c	F	6.800	5.194	1.606	∞	input port clock
Path 7	∞	3	2	8	x	a6	6.797	5.191	1.606	∞	input port clock
Path 8	∞	3	2	7	c	B	6.794	5.189	1.606	∞	input port clock
Path 9	∞	3	2	7	c	A	6.792	5.186	1.606	∞	input port clock
Path 10	∞	3	2	8	z	a1	6.789	5.184	1.606	∞	input port clock

## Part F

The maximum delay in Implementation is from z to a6 of 12.565 ns.

The path is not the same as in the synthesis report and neither is the max delay.

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	3	2	8	z	a6	12.565	5.400	7.166	∞	input port clock
↳ Path 2	∞	3	2	7	a	A	10.419	5.409	5.010	∞	input port clock
↳ Path 3	∞	3	2	8	z	a3	10.310	5.433	4.877	∞	input port clock
↳ Path 4	∞	3	2	8	z	a0	10.223	5.414	4.810	∞	input port clock
↳ Path 5	∞	3	2	7	a	B	10.115	5.157	4.958	∞	input port clock
↳ Path 6	∞	3	2	7	a	F	10.100	5.398	4.702	∞	input port clock
↳ Path 7	∞	3	2	8	z	a1	10.093	5.184	4.910	∞	input port clock
↳ Path 8	∞	3	2	7	a	D	9.621	5.382	4.240	∞	input port clock
↳ Path 9	∞	3	2	8	z	a2	9.477	5.222	4.255	∞	input port clock
↳ Path 10	∞	3	2	8	z	a4	9.444	5.198	4.246	∞	input port clock

## Part G

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	8	0	63400	0.01
LUT as Logic	8	0	63400	0.01
LUT as Memory	0	0	19000	0.00
Slice Registers	0	0	126800	0.00
Register as Flip Flop	0	0	126800	0.00
Register as Latch	0	0	126800	0.00
F7 Muxes	0	0	31700	0.00
F8 Muxes	0	0	15850	0.00

Name	Direction	Neg Diff Pair	Package Pin	Fixed	Bank	I/O Std	Vcco	Vref	Drive Strength	Slew Type
All ports (23)										
Scalar ports (23)										
a	IN		J15	✓	15	LVC MOS33*	3.300			
b	IN		L16	✓	14	LVC MOS33*	3.300			
c	IN		M13	✓	14	LVC MOS33*	3.300			
d	IN		R15	✓	14	LVC MOS33*	3.300			
x	IN		U12	✓	14	LVC MOS33*	3.300			
y	IN		U11	✓	14	LVC MOS33*	3.300			
z	IN		V10	✓	14	LVC MOS33*	3.300			
A	OUT		T10	✓	14	LVC MOS33*	3.300	12	✓	SLOW
a0	OUT		J17	✓	15	LVC MOS33*	3.300	12	✓	SLOW
a1	OUT		J18	✓	15	LVC MOS33*	3.300	12	✓	SLOW
a2	OUT		T9	✓	14	LVC MOS33*	3.300	12	✓	SLOW
a3	OUT		J14	✓	15	LVC MOS33*	3.300	12	✓	SLOW
a4	OUT		P14	✓	14	LVC MOS33*	3.300	12	✓	SLOW
a5	OUT		T14	✓	14	LVC MOS33*	3.300	12	✓	SLOW
a6	OUT		K2	✓	35	LVC MOS33*	3.300	12	✓	SLOW
a7	OUT		U13	✓	14	LVC MOS33*	3.300	12	✓	SLOW
B	OUT		R10	✓	14	LVC MOS33*	3.300	12	✓	SLOW
C	OUT		K16	✓	15	LVC MOS33*	3.300	12	✓	SLOW
D	OUT		K13	✓	15	LVC MOS33*	3.300	12	✓	SLOW
DP	OUT		H15	✓	15	LVC MOS33*	3.300	12	✓	SLOW
E	OUT		P15	✓	14	LVC MOS33*	3.300	12	✓	SLOW
F	OUT		T11	✓	14	LVC MOS33*	3.300	12	✓	SLOW
G	OUT		L18	✓	14	LVC MOS33*	3.300	12	✓	SLOW