

Name: Ayesha Ahmad


EE-272L Digital Systems Design

Reg. No.: 2021-EE-052

Marks Obtained: _____

Lab Manual 2

Combinational Circuit Simulation

 

Question 1

Part A

A	B	C	$O = \bar{C}$	$R = P = A + B$	$Q = AB$	$S = \bar{Q}\bar{R}$	$X = O \oplus P$	$Y = P \oplus S$
0	0	0	1	0	0	1	1	1
0	0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	1	1	0
1	0	0	1	1	0	1	0	0
1	0	1	0	1	0	1	1	0
1	1	0	1	1	1	0	0	1
1	1	1	0	1	1	0	1	1

Part B

The errors found in Listing 4 include:

1. Line 4: A ';' (semicolon) was used but a ',' (comma) should have been used.
2. Line 9: A ';' (semicolon) was missing at the end of the line.
3. Line 10: The '&' (AND symbol) was missing between 'c' and '(a ^ b)'.

The errors found in Listing 5 include:

1. Line 8: Missing instance name in initiation of module.
2. Line 19: Logic a, b, and c are not defined here so it is incorrect. Instead use a1, b1 and c1.
3. Line 21: c is used here instead of c1.
4. Line 25: b is used here instead of b1.
5. Line 31: a is used here instead of a1.
6. Line 36: Missing 'end'

Part C

Corrected code of Listing 4 is:

```
module full_adder(
    input logic a,
    input logic b,
    input logic c,
    output logic sum,
    output logic carry
);

    assign sum = (a ^ b) ^ c;
    assign carry = (a & b) | (c & (a ^ b));

endmodule
```

Corrected code of Listing 5 is:

```
module full_adder_tb();
    logic a1;
    logic b1;
    logic c1;
    logic sum1;
    logic carry1;

    a1 = 1; b1 = 1; c1 = 1;
    #10;
    $stop;
end
endmodule

full_adder UUT(
    .a(a1),
    .b(b1),
    .c(c1),
    .sum(sum1),
    .carry(carry1)
);

initial
begin
    // Provide different combinations of the
    // inputs to check validity of code
    a1 = 0; b1 = 0; c1 = 0;
    #10;
    a1 = 0; b1 = 0; c1 = 1;
    #10;
    a1 = 0; b1 = 1; c1 = 0;
    #10;
    a1 = 0; b1 = 1; c1 = 1;
    #10;
    a1 = 1; b1 = 0; c1 = 0;
    #10;
    a1 = 1; b1 = 0; c1 = 1;
    #10;
    a1 = 1; b1 = 1; c1 = 0;
    #10
end
```

Question 2

System Verilog code of given circuit is:

```
`timescale 1ns/10ps

module task1(output logic x,y,
input logic a,b,c
);
wire o,p,q,r,s;

not n1(o,c);
or o1(p,a,b);
or o2(r,a,b);
and a1(q,a,b);
nand na1(s,q,r);
xor xo1(x,o,p);
xor xo2(y,p,s);

endmodule
```

Question 3

Test Bench code of given circuit is:

```
`timescale 1ns/10ps

module task1_tb;
logic a1;
logic b1;
logic c1;
logic x1;
logic y1;

localparam period = 10;
task1 UUT(
.a(a1),
.b(b1),
.c(c1),
.x(x1),
.y(y1)
);

initial //initial block executes only once
begin
// Provide different combinations of the
inputs to check validity of code
a1 = 0; b1 = 0; c1 = 0;
#period;
a1 = 0; b1 = 0; c1 = 1;
#period;
a1 = 0; b1 = 1; c1 = 0;
#period;
a1 = 0; b1 = 1; c1 = 1;
#period;
a1 = 1; b1 = 0; c1 = 0;
#period;
a1 = 1; b1 = 0; c1 = 1;
#period;
a1 = 1; b1 = 1; c1 = 0;
#period;
a1 = 1; b1 = 1; c1 = 1;
#period;
$stop;
end

initial
begin
/*the following system task will print
out the signal values
every time they change on the Transcript
Window */
$monitor("y=%b, x=%b, a=%b, b=%b,
c=%b", y1,x1,a1,b1,c1);
end

endmodule
```

Question 4

